
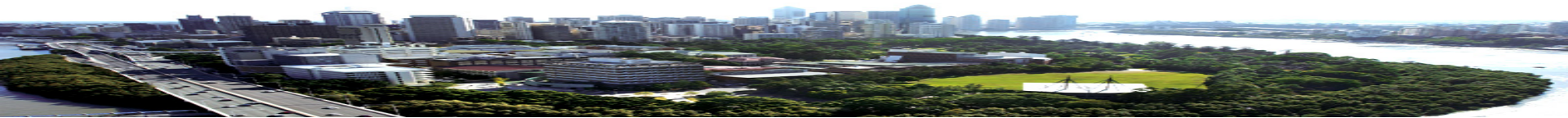


ENB 350 Real-time Computer based systems

Pre-requisite knowledge Test

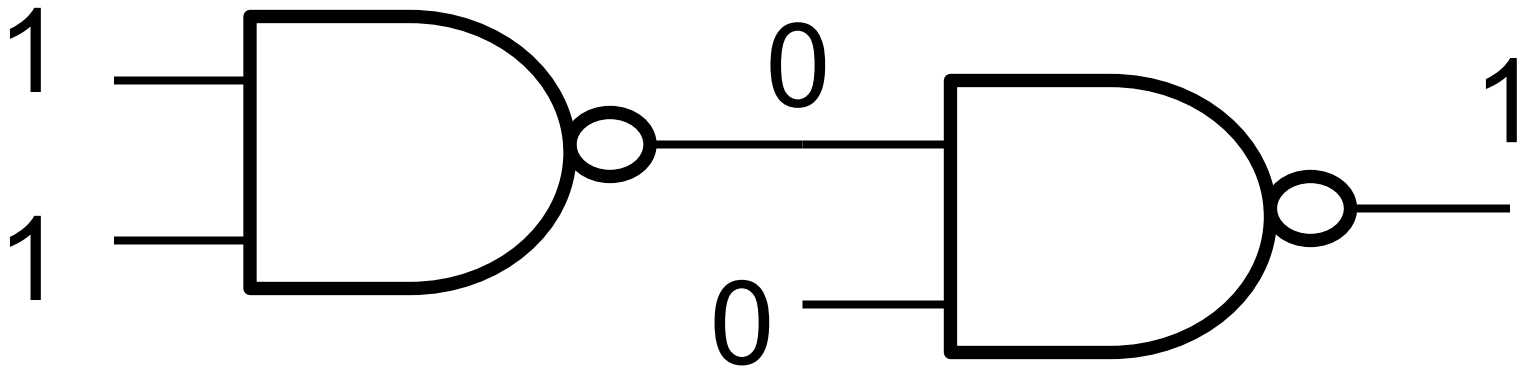

What is the output?



What is it enough for?

The output current from a typical CMOS microcontroller digital output line is enough for

- An LED ? **Yes** or No
- A small dc motor ? Yes or **No**
- A solenoid ? Yes or **No**




Complete the Truth Table

- For a full adder.

A	B	Carry In	Sum	Carry out
0	0	0	0	0
0	1	1	0	1
1	0	0	1	0
1	1	1	1	1



What is the next state?

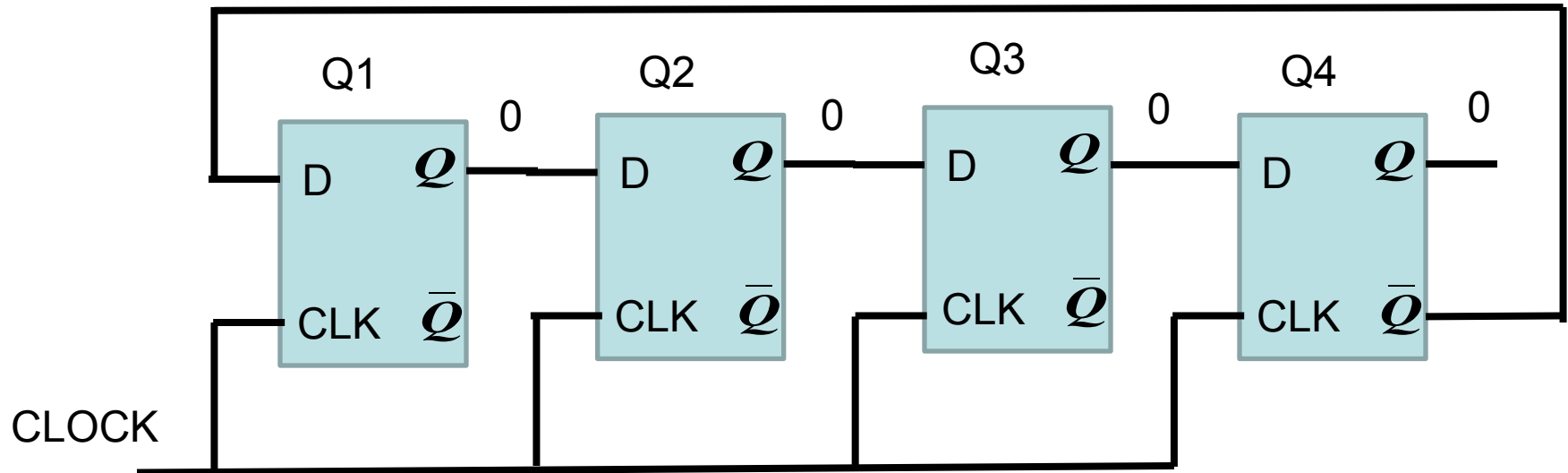

Present state Q1 Q2 Q3 Q4 is 0 0 0 0

Next state = 1 0 0 0



What is in a CPU?

The central processing unit (CPU) of a microprocessor comprises of

- Arithmetic logic unit (Yes or No)
- Control logic (Yes or No)
- System clock (Yes or No)
- Memory (Yes or No)
- Registers (Yes or No)



A program counter keeps

- A. data that needs to be incremented by 1
- B. the size of the program
- C. the number of running programs
- D. the address of the next instruction ✓
- E. None of the above



What is this number?

In 8 bit 2s complement notation it is

11111111

In decimal notation it is

-1




Are these key words in ANSI C?

for	✓
if	✓
waitfor	
while	✓
printf	
costate	
end	



The & operator in C is

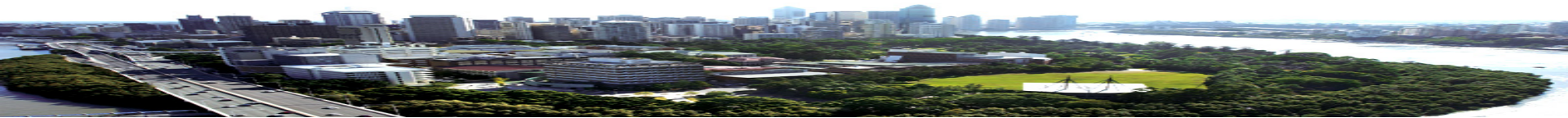- A. addition
- B. logical AND
- C. bitwise AND ✓
- D. concatenation
- E. None of the above



What is the output?

```
#include <stdio.h>
void main()
{
extern void swap();
int a,b;
a =10; b=20;
swap(a,b);
printf("a = %d\n",a);
exit(0);
}
```

```
void swap(int x, int y)
{
int temp;
temp = x;
x = y;
y = temp;
}
```

a = 10

